


# A Homebrew Digimode- Transceiver

**Henning Paul DC4HP**

**10.10.2023**

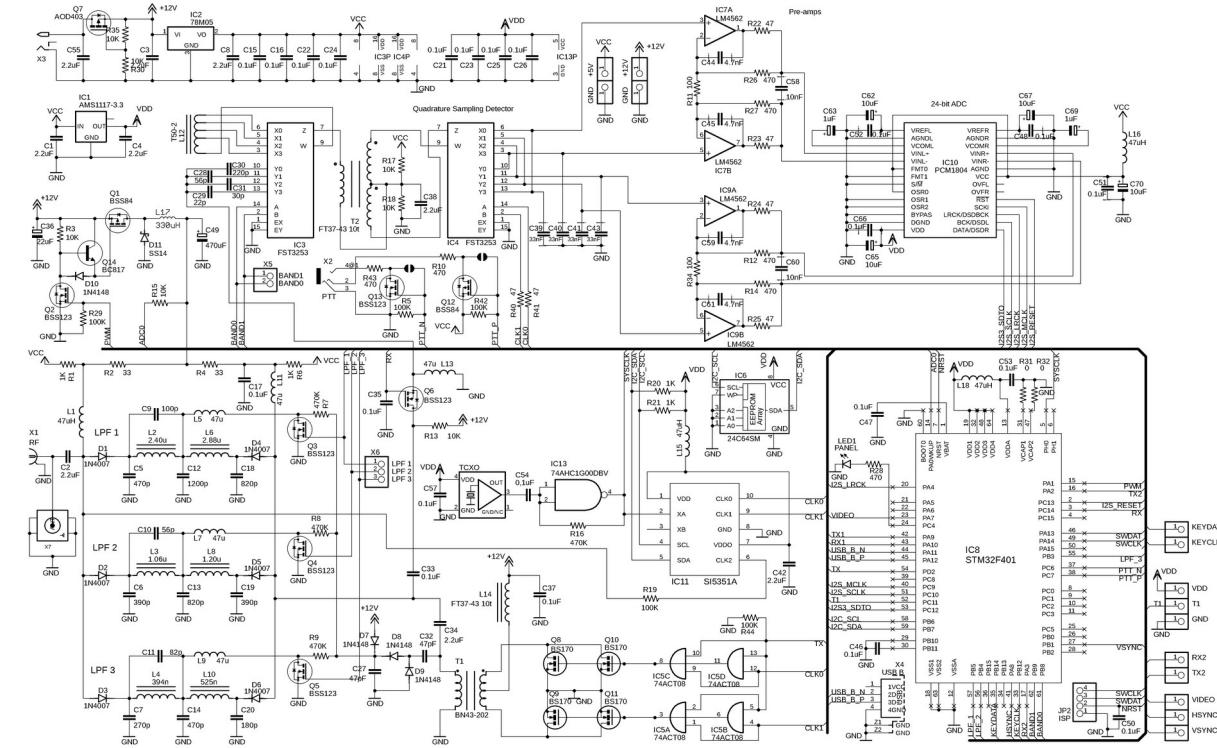
# Motivation

- Was pointed at QDX by fellow ham
- Schematics available online



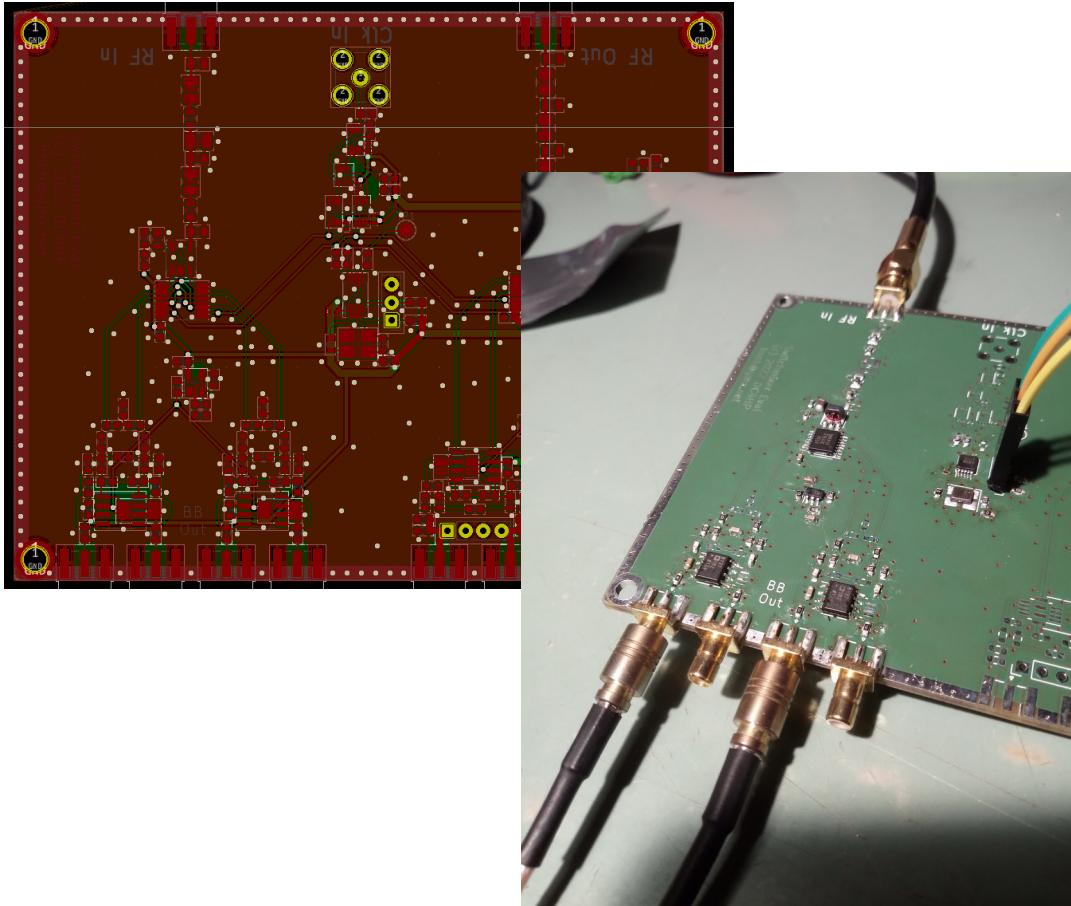
# H-mode mixer

- Gained interest in workings of quadratur H-mode mixer
- Layouted experimenter board to study it



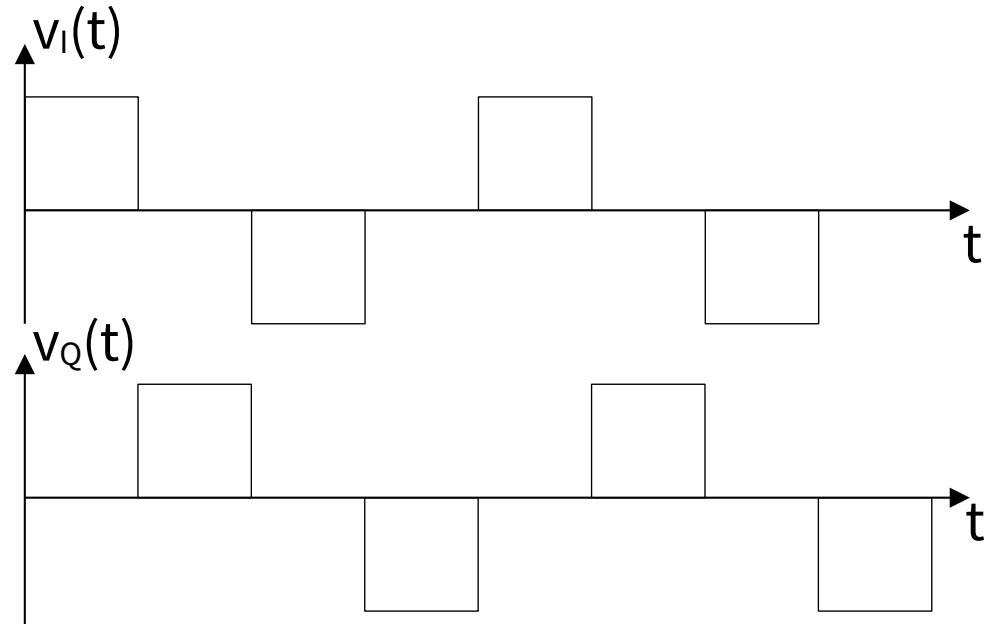
# H-mode mixer

- Mode of operation:
  - Received HF is switched onto I and Q receive path with alternating sign in a round-robin fashion



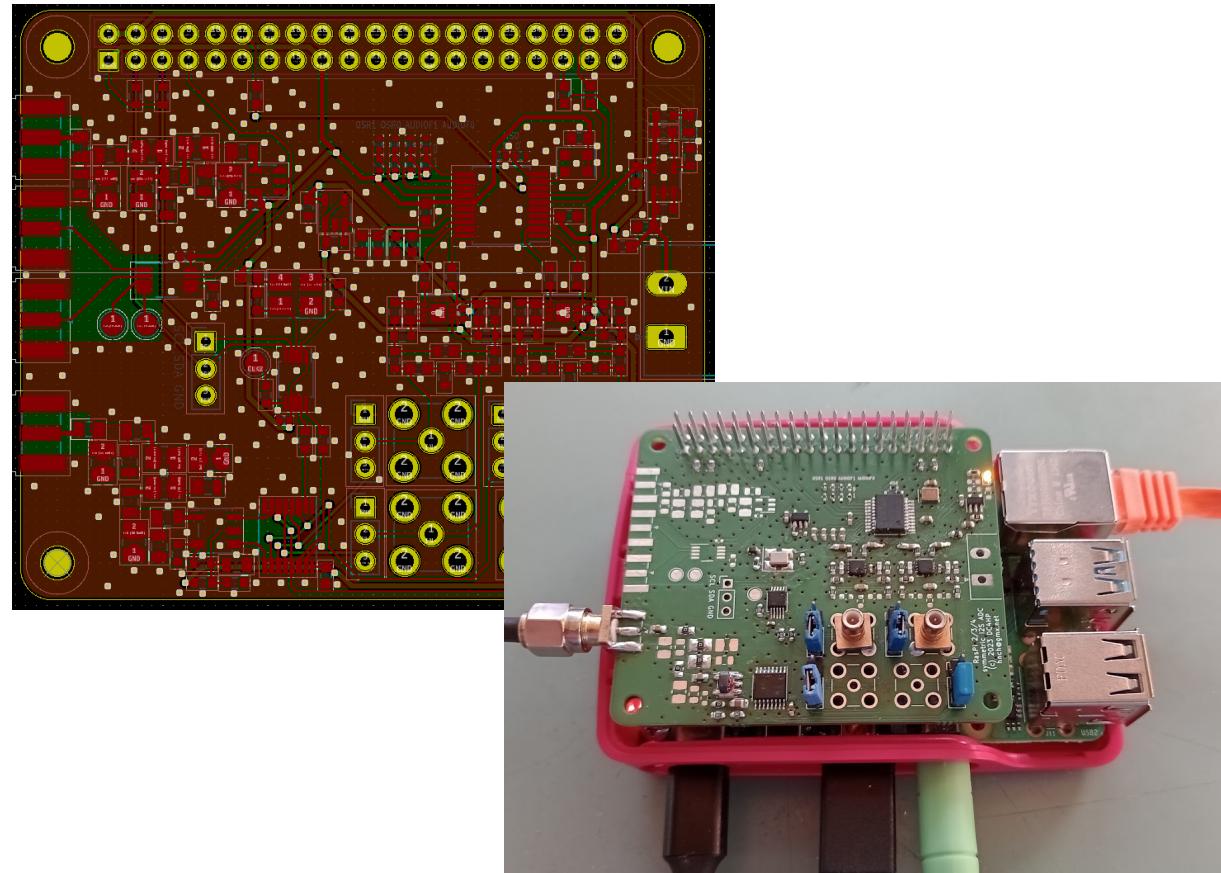
# Raspberry Pi Hat

- After successful tests with a USB audio adapter I developed a hat for the Raspberry Pi using a 192kHz/24bit ADC



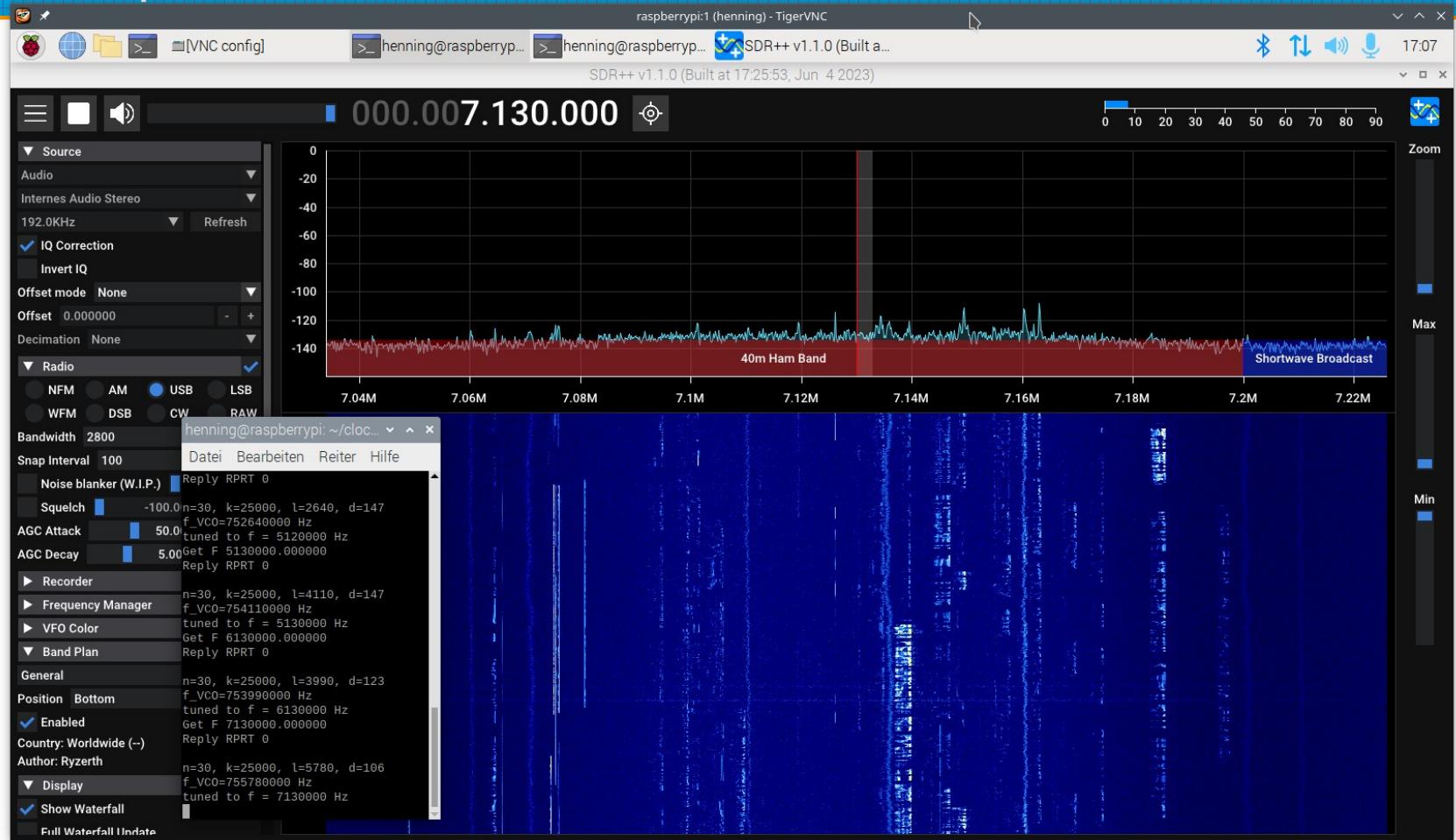
# Receiver performance

- Fixed gain (20dB in ADC driver only)
- No HF filtering




# Receiver performance

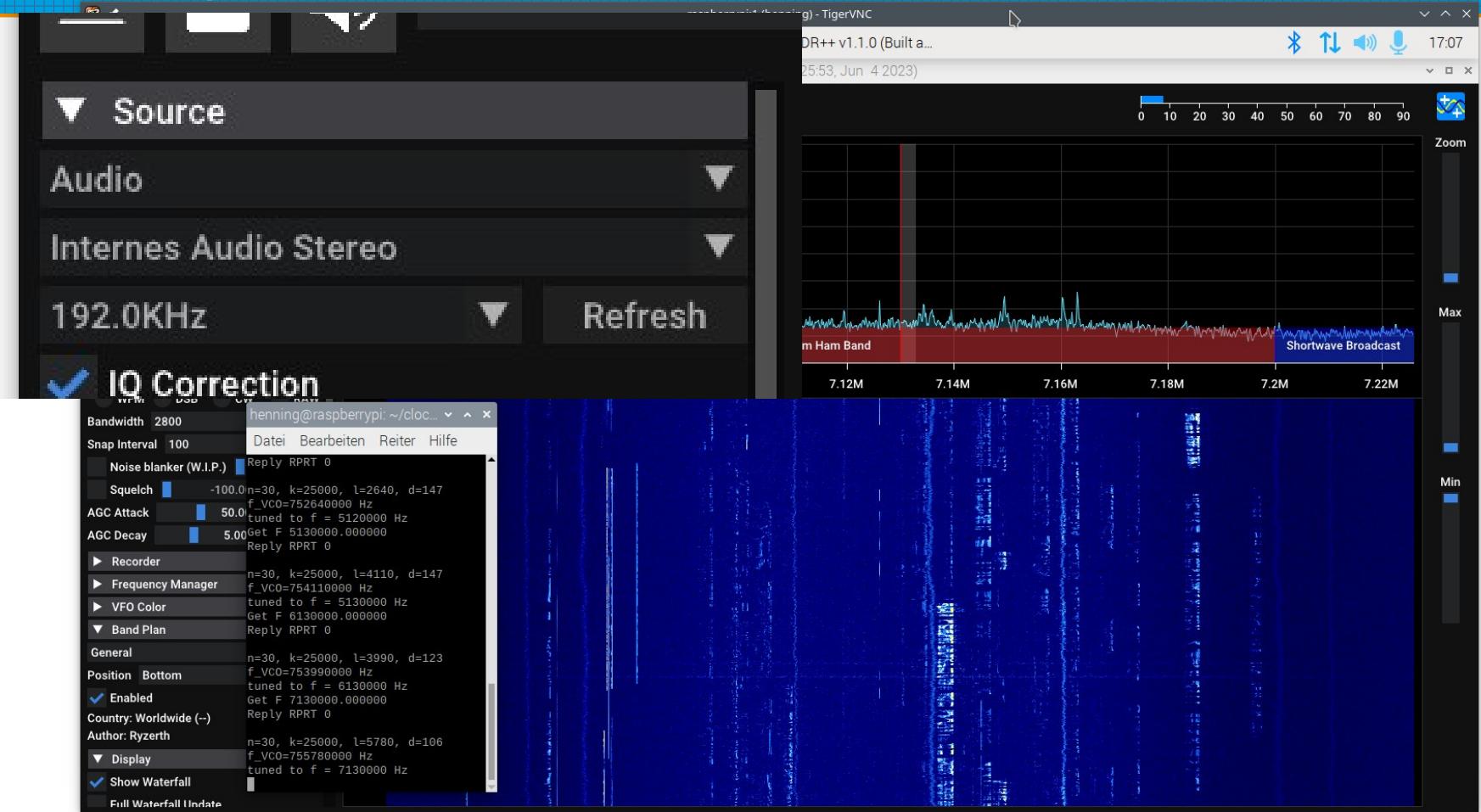


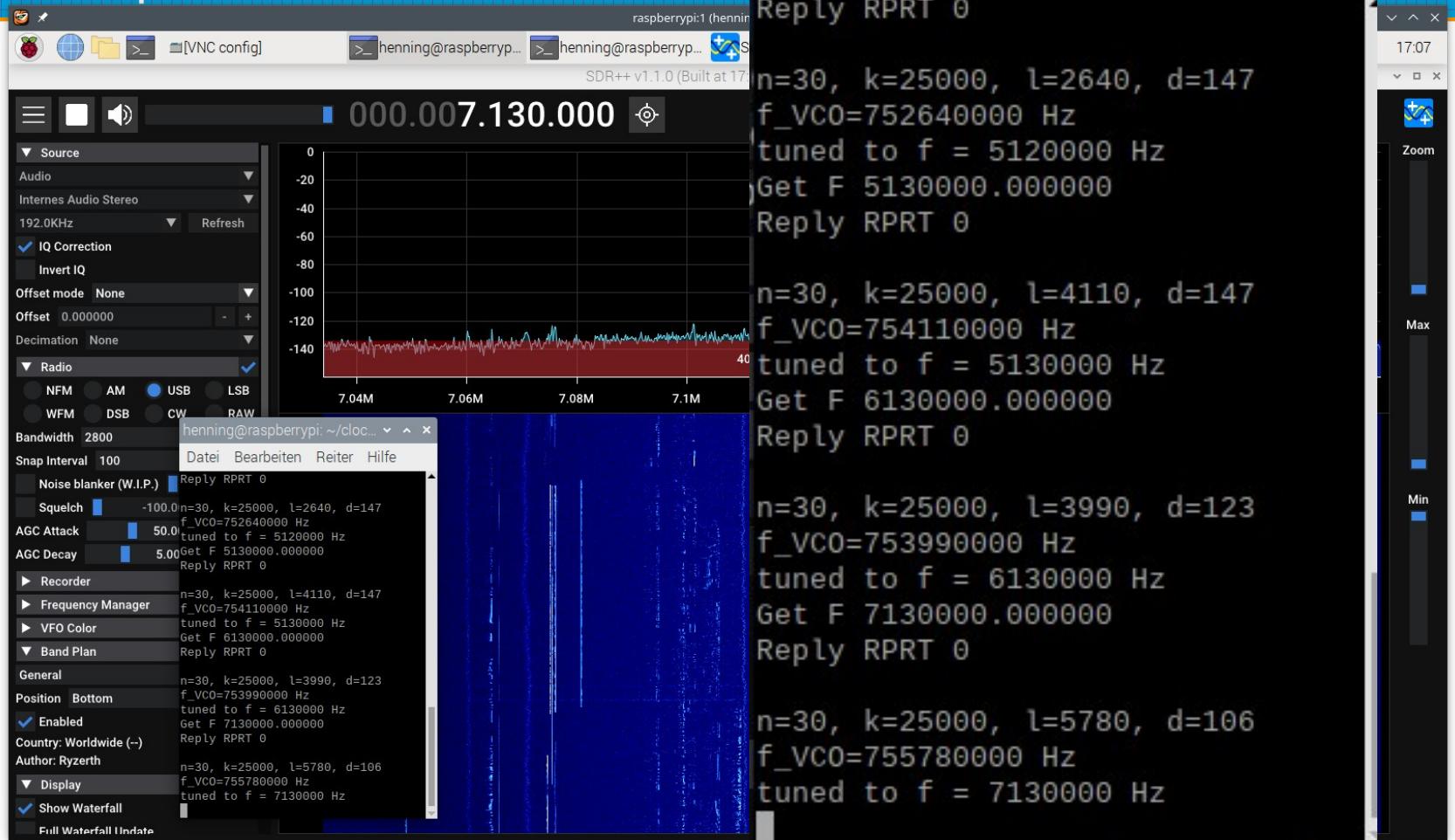
# Receiver performance

- Python script emulating rigctl to control Si5351A synth


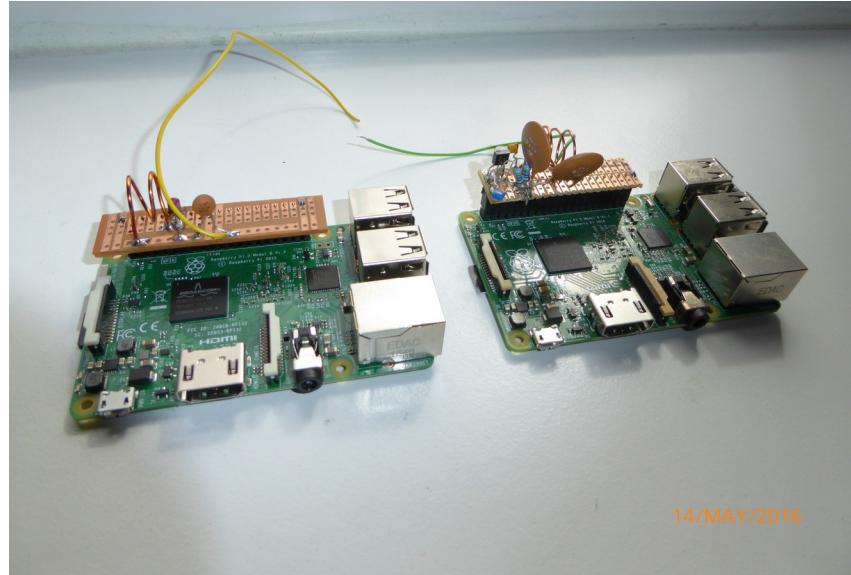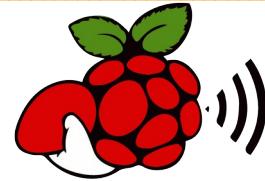
# Transmit signal generation

- rpitx by Evariste F5OEO  
(<https://github.com/F5OEO/rpitx>)
- Clock synthesizer of Raspberry Pi is abused to generate arbitrary clock signals on Pin 7
- Originally only FM/FSK possible - but since RPi 2 also AM, SSB and OFDM




14/MAY/2016


Photo: Gerald DL5BBN (TU Berlin), 2016

# Transmit signal generation

- rpitx wave forms

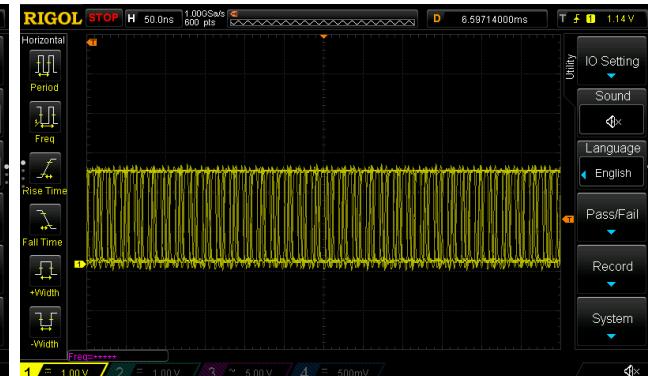

- NBFM on 10m

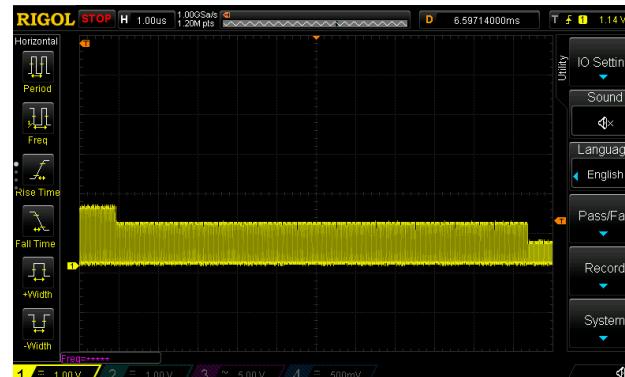


- SSB on 10m:

- Simultaneous FM and AM to create SSB


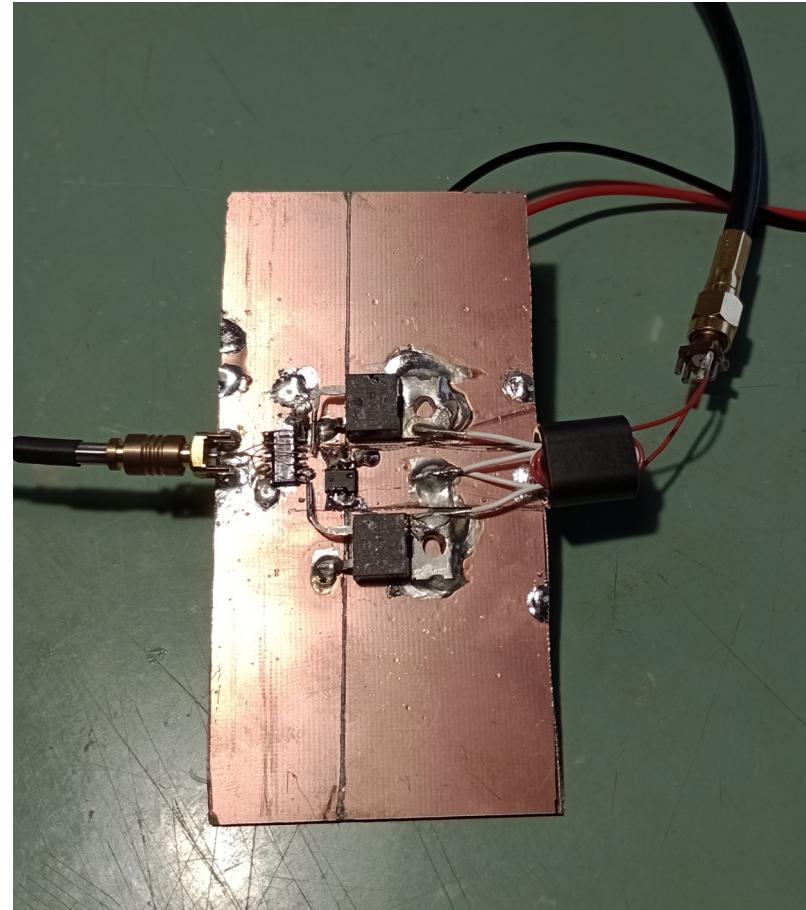
# Power amplifier

- Output signal of Raspberry Pi is 3.3V logic level (at least for FSK):
- Option 1: Filter and feed into (linear) HF PA
- Option 2: Use digital (switching) PA
- Experiments using circuit derived from QDX (but with stronger MOSFETs)



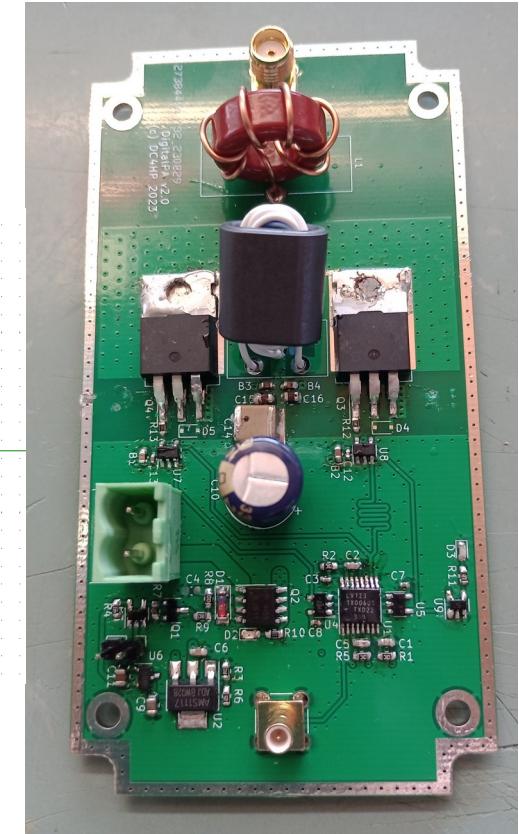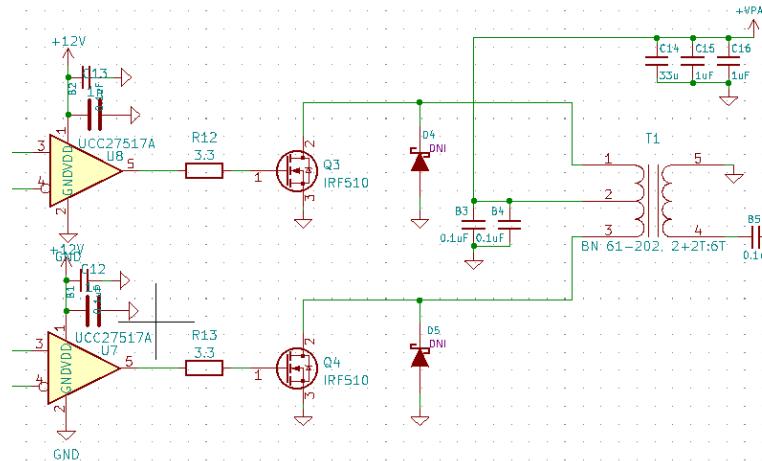
# Power amplifier

- Final circuit:
  - 4A gate driver
  - High side PMOS to switch on PA
  - Under frequency lockout (500kHz) to avoid destruction of transistors by DC levels




# Power amplifier

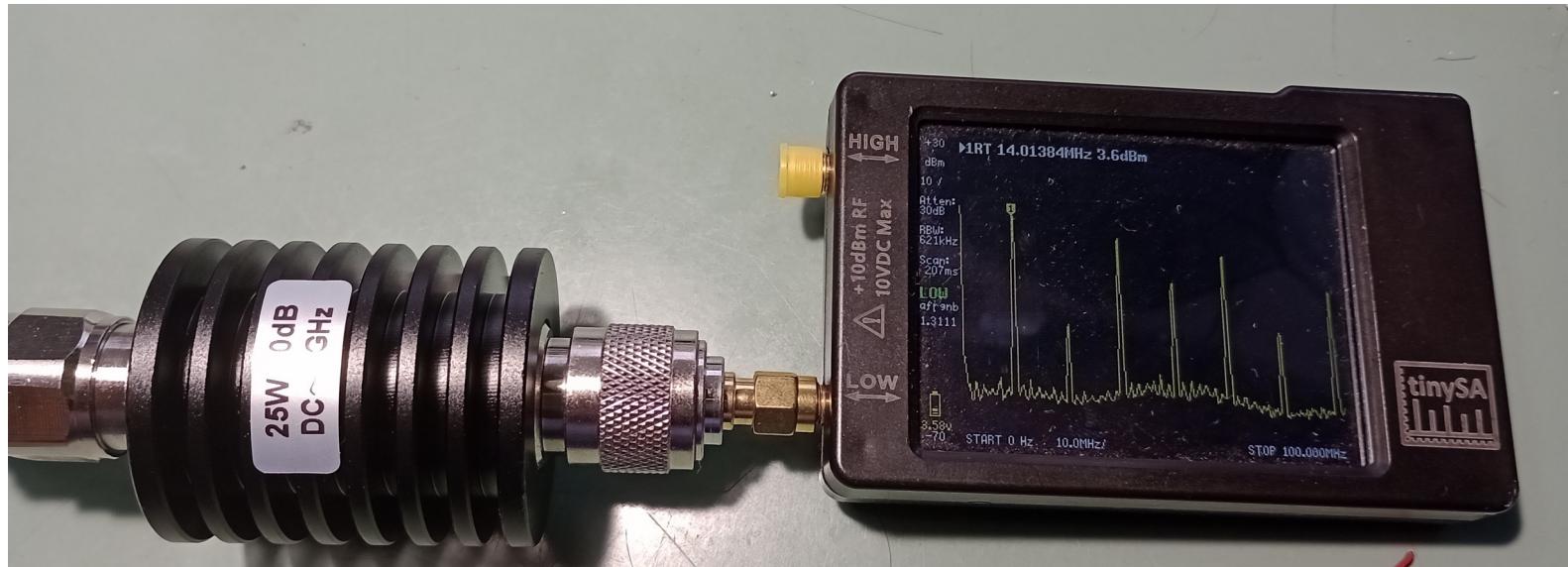- 43.6dBm (~22W) in the fundamental on 20m with 14V supply voltage (measured before low pass)



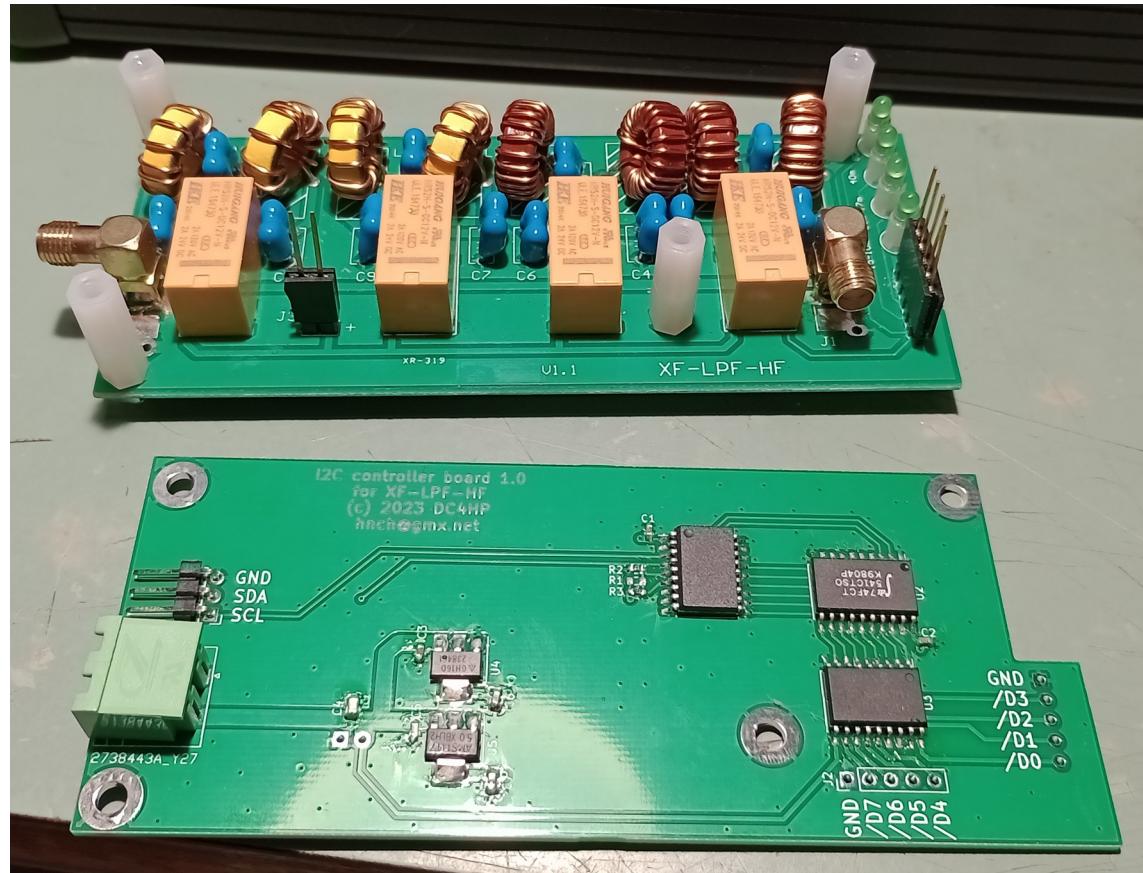
# Power amplifier

- Filtering using XF-LPF-HF from AliExpress
- Controlled via I2C using self-designed controller board




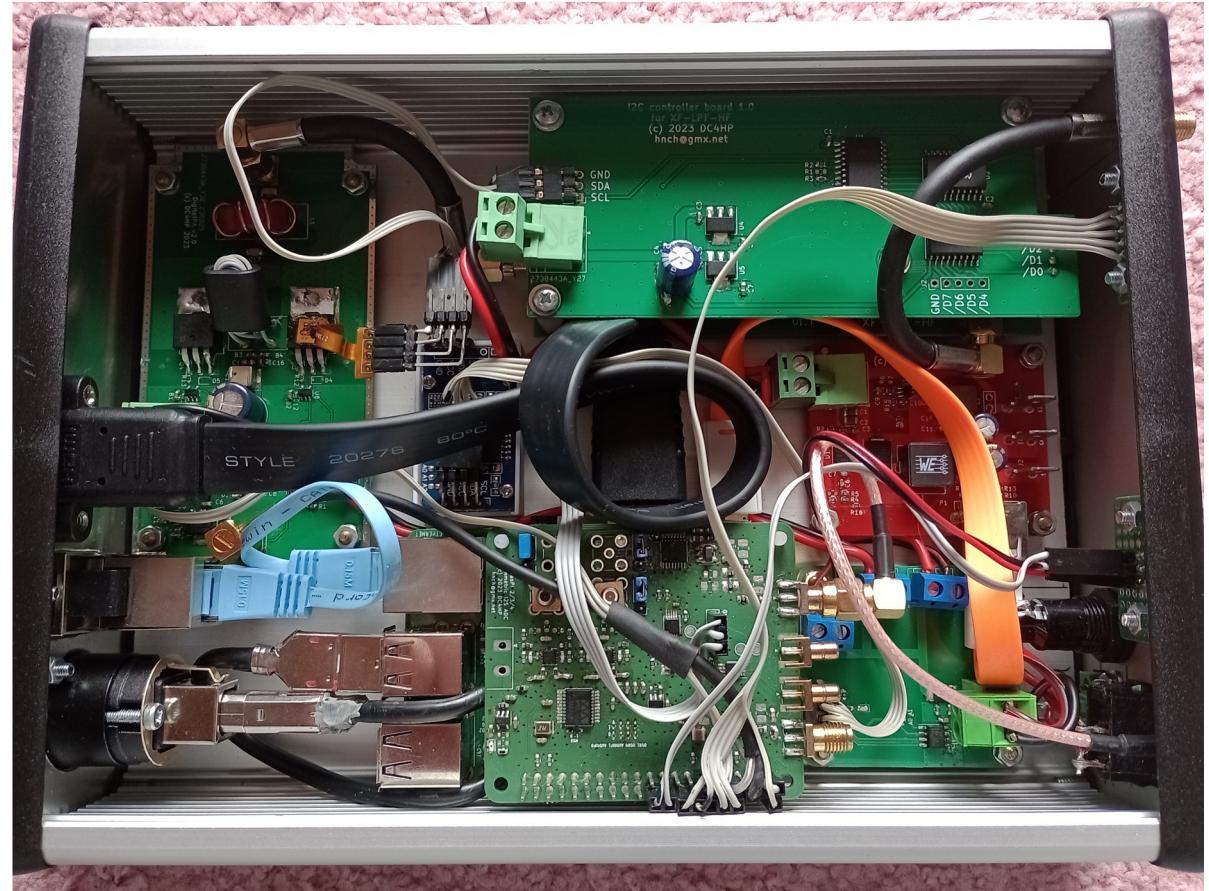
# Putting it all together

- LAN, USB and HDMI routed to front panel
- I2C RTC and serial port für GPS receiver
- 5V for RPi generated by self layouted DC/DC board


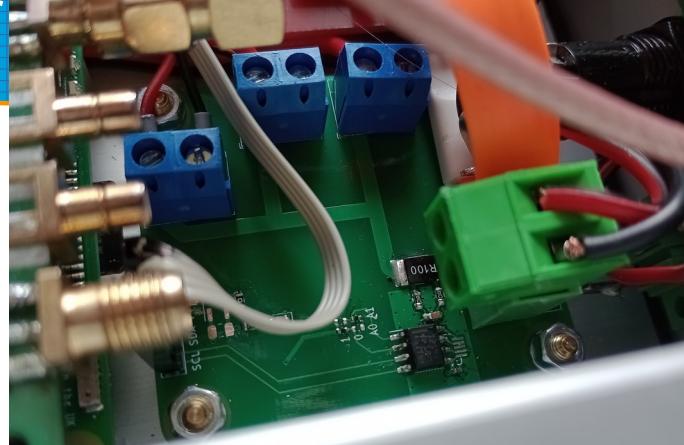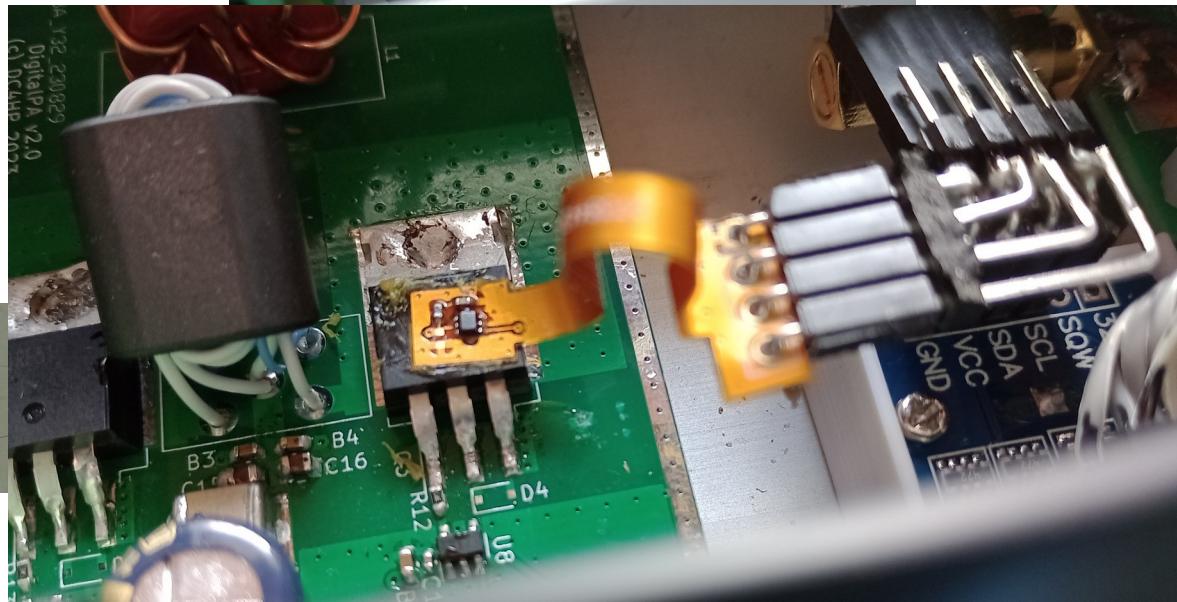
# Putting it all together

- Measurement of input current and voltage using self-designed board
- Measurement of PA temperature using self-designed flex board



# Putting it all together

- ATU-100 antenna tuner and Rx/Tx switch externally
- Supplied from SLA or LiFePo4 battery




# The software


- Python / GNU Radio under Linux on the Raspberry Pi
- GNU Radio Flowgraph for Rx:
  - Capture from I2S ADC; LPF at 2.9kHz; Output to virtual sound card
- GNU Radio Flowgraph for Tx:
  - Capture from virtual sound card; SSB modulation; Output to rpitx-Block  
(<https://github.com/jmfriedt/gr-rpitx>)
- Python script emulated rigctld
  - Controls Rx mixer's Si5351A via I2C
  - Parametrizes Tx flow graph via ZMQ
  - Controls output LPF via I2C
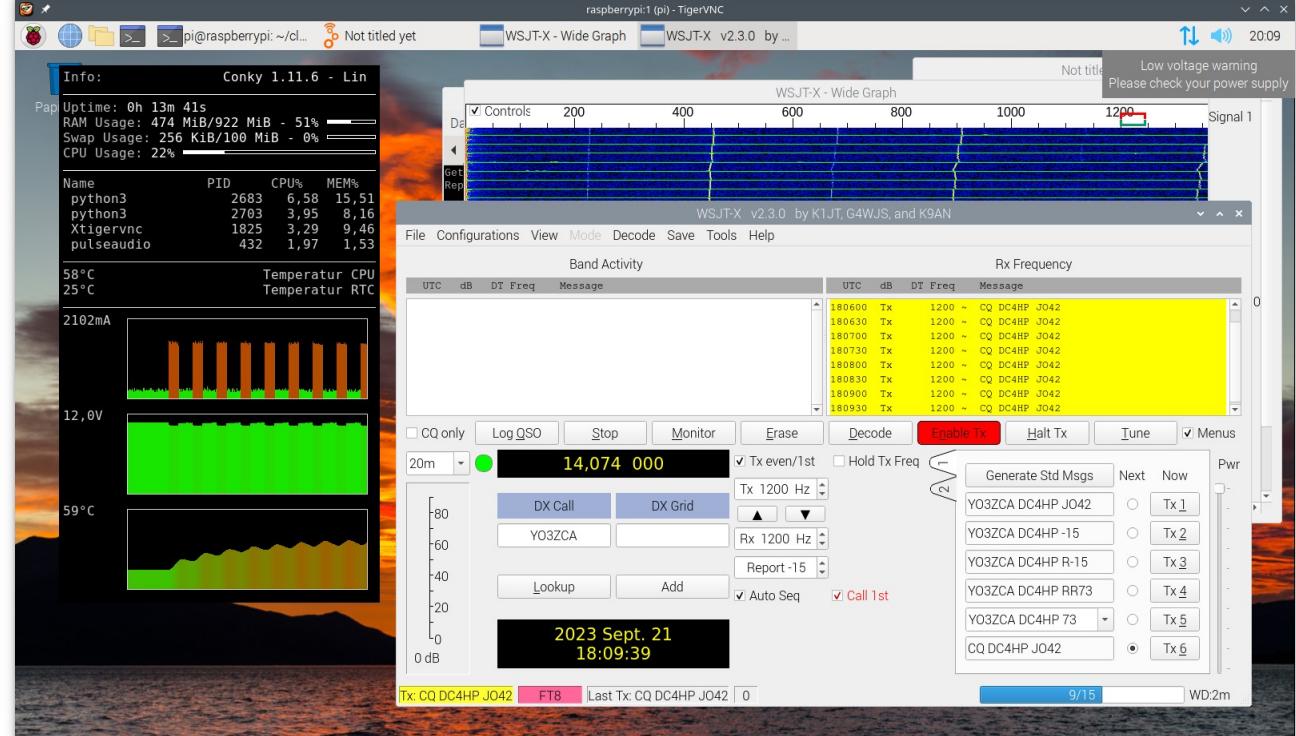
# The software


- Current, voltage and temperature sensors available via standard Linux sensors API → use any tool you like for display



# Impressions from the practical use

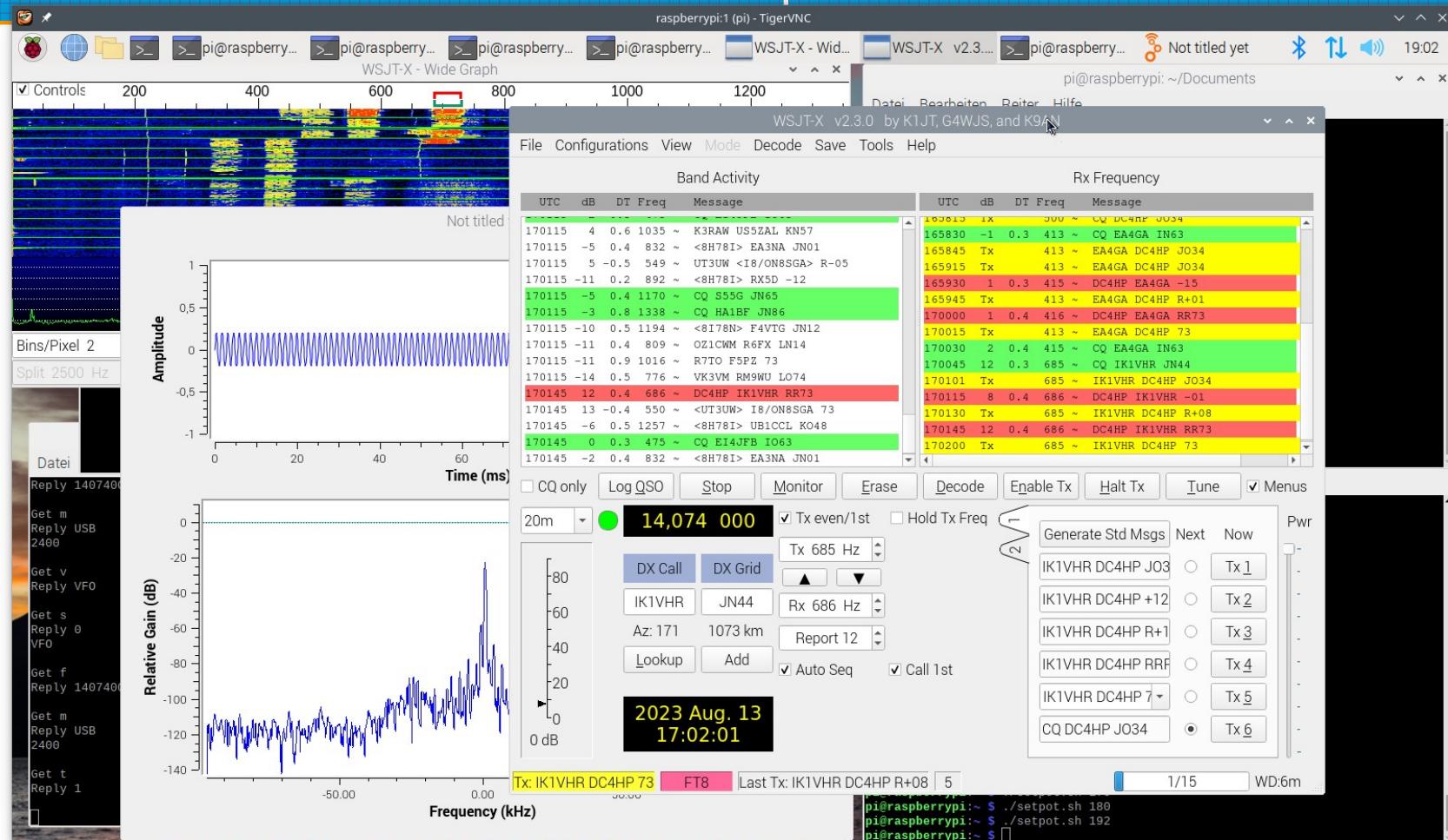

# Impressions from the practical use

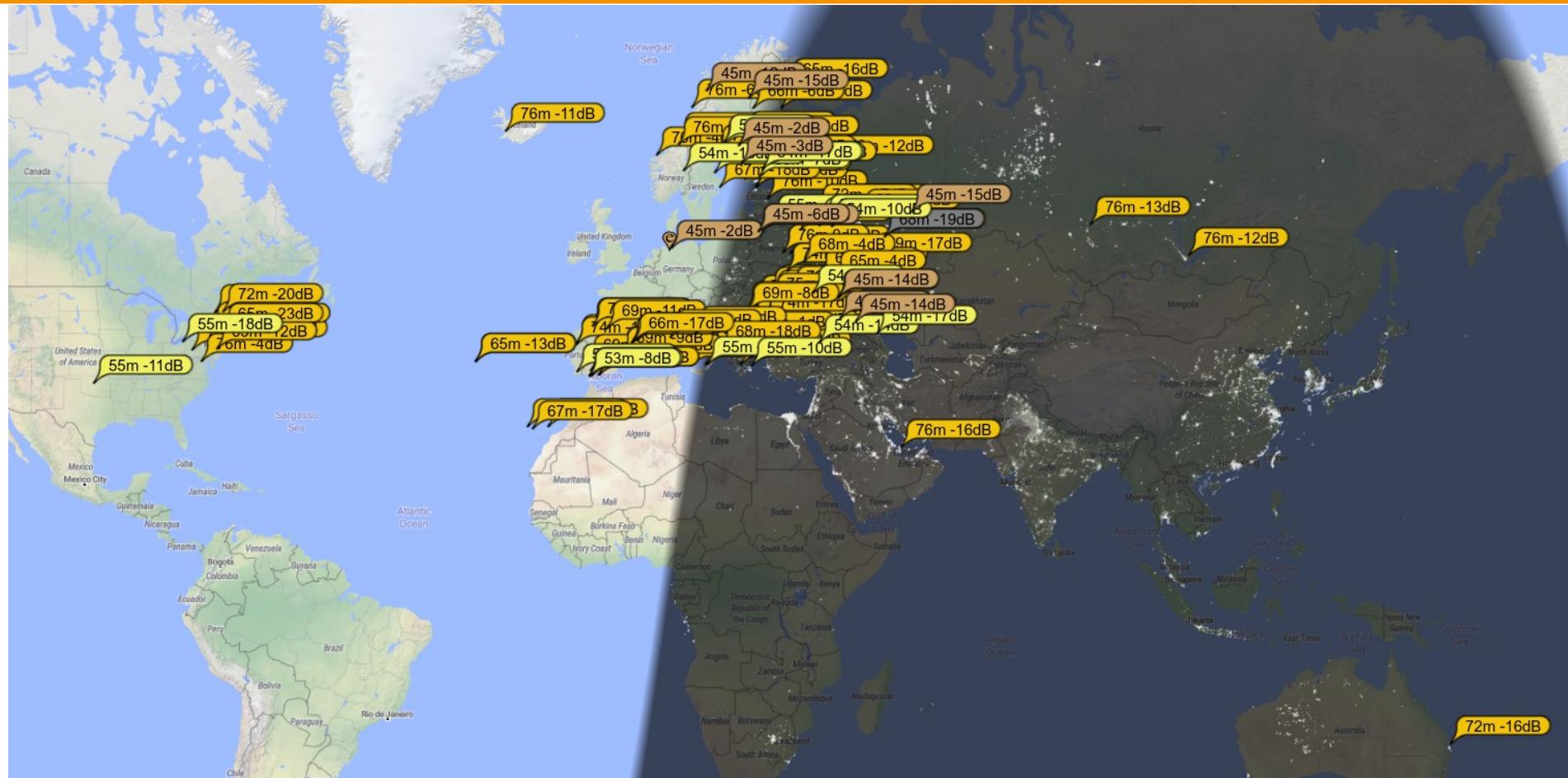

**Thank you very much!**